

Logic and PLC Ladder diagrams

Dr Diarmuid Ó Briain

Learning objectives

- Logic Circuits
- PLC Operating Principles
- PLC Control Features
- Ladder Diagrams.



2

Logic Circuits



IEC	ANSI	Description	Boolean
		The AND gate output is at logic 1 when, and only when all its inputs are at logic 1, otherwise the output is at logic 0.	$X = A \cdot B$
		The OR gate output is at logic 1 when one or more of its inputs are at logic 1. If all the inputs are at logic 0, the output is at logic 0.	$X = A + B$
		The NAND Gate output is at logic 0 when, and only when all its inputs are at logic 1, otherwise the output is at logic 1.	$X = \overline{A \cdot B}$
		The NOR gate output is at logic 0 when one or more of its inputs are at logic 1. If all the inputs are at logic 0, the output is at logic 1.	$X = \overline{A + B}$
		The XOR gate output is at logic 1 when one and ONLY ONE of its inputs is at logic 1. Otherwise the output is logic 0.	$X = A \oplus B$
		The XNOR gate output is at logic 0 when one and ONLY ONE of its inputs is at logic 1. Otherwise the output is logic 1. (It is similar to the XOR gate, but its output is inverted).	$X = \overline{A \oplus B}$
		The NOT gate output is at logic 0 when its only input is at logic 1, and at logic 1 when its only input is at logic 0. For this reason it is often called an INVERTER.	$X = \overline{A}$

- International Electrotechnical Commission (IEC)
- American National Standards Institute (ANSI)

3

Logic Circuits – N/OT (Inverter)




Truth table

A	X	$\overline{A}$
F	T	
T	F	

Binary Truth table

A	X	$\overline{A}$
0	1	
1	0	


$\overline{A}$ means N/OT A

 

- Bulb lit when switch is not pressed.
- Bulb is not lit when switch is pressed.
- "X" is the opposite state to "A".

4

Logic Circuits - AND

 


Truth table

A	B	X A.B
F	F	F
F	T	F
T	F	F
T	T	T

Binary Truth table

A	B	X A.B
0	0	0
0	1	0
1	0	0
1	1	1

A.B means "A" AND "B"

 

- Bulb will only light if "A" AND "B" are depressed together.

5

Logic Circuits - NAND




Truth table

A	B	X $\overline{A.B}$
F	F	T
F	T	T
T	F	T
T	T	F

Binary Truth table

A	B	X A.B
0	0	1
0	1	1
1	0	1
1	1	0


$\overline{A.B}$ means N/OT "A" AND "B"

 

- Bulb will always light unless "A" AND "B" are depressed together.

6

Logic Circuits - OR

 


Truth table

A	B	X A+B
F	F	F
F	T	T
T	F	T
T	T	T

Binary Truth table

A	B	X A+B
0	0	0
0	1	1
1	0	1
1	1	1


A+B means "A" OR "B"

 

- Bulb will light if either "A" OR "B" are depressed.

7

Logic Circuits - NOR

 


Truth table

A	B	X $\overline{A+B}$
F	F	T
F	T	F
T	F	F
T	T	F

Binary Truth table

A	B	X A+B
0	0	1
0	1	0
1	0	0
1	1	0


$\overline{A+B}$ means "A" N/OR "B"

 

- Bulb will light unless either "A" or "B" or both are depressed.

8

Logic Circuits - XOR

 


Truth table

A	B	X $A \oplus B$
F	F	F
F	T	T
T	F	T
T	T	F

Binary Truth table

A	B	X $A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0

$A \oplus B$ means "A" XOR "B"

 


- Bulb will light if either "A" OR "B" are depressed.

9

N/OT gates using NAND gates



N/OT

 


10


N/OT gates using NAND gates



N/OT

 

AND

 

Binary Truth table


A	B	X A.B
0	0	0
0	1	0
1	0	0
1	1	1

11


N/OT gates using NAND gates



N/OT

 


AND

 




Binary Truth table

A	B	X A.B
0	0	0
0	1	0
1	0	0
1	1	1

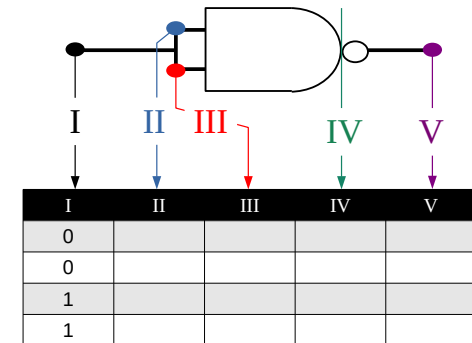




12

N/OT gates using NAND gates

   




13

N/OT gates using NAND gates

  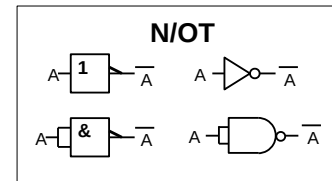




14

N/OT gates using NAND gates

   



15

N/OT gates using NAND gates

   

16

N/OT gates using NAND gates

  


17


AND gates using NAND gates



AND

 

AND from NAND gates

 


18


AND gates using NAND gates



AND

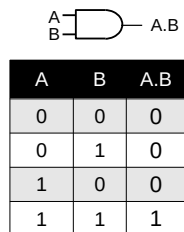

AND from NAND gates

 


19


AND gates using NAND gates



AND

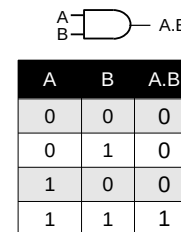

AND from NAND gates

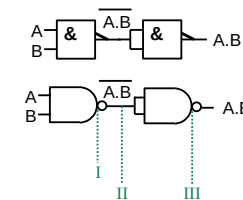


20

AND gates using NAND gates




AND

 

A	B	A.B
0	0	0
0	1	0
1	0	0
1	1	1

AND from NAND gates

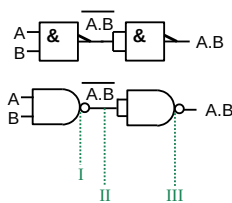


A	B	I	II	III	A.B
0	0	0	1	1	
0	1	0	1	1	
1	0	0	1	1	
1	1	1	0	0	

21

AND gates using NAND gates




AND

 

A	B	A.B
0	0	0
0	1	0
1	0	0
1	1	1

AND from NAND gates

 


A	B	I	II	III	A.B
0	0	0	1	1	0
0	1	0	1	1	0
1	0	0	1	1	0
1	1	1	0	0	1

22

OR gates using NAND gates




OR

 

A	B	A+B
0	0	0
0	1	1
1	0	1
1	1	1

OR from NAND gates

 

A	I	$\bar{A}$	B	II	$\bar{B}$	III	A+B
0			0				
0			1				
1			0				
1			1				

23

OR gates using NAND gates




OR



A	B	A+B
0	0	0
0	1	1
1	0	1
1	1	1

OR from NAND gates

 


A	I	$\bar{A}$	B	II	$\bar{B}$	III	A+B
0	0	1	0				
0	0	1	1				
1	1	0	0				
1	1	0	1				

24

OR gates using NAND gates




OR

 

A	B	A.B
0	0	0
0	1	1
1	0	1
1	1	1

OR from NAND gates

 

A	I	$\bar{A}$	B	II	$\bar{B}$	III	A+B
0	0	1	0	0	1		
0	0	1	1	1	0		
1	1	0	0	0	1		
1	1	0	1	1	0		

25

OR gates using NAND gates




OR



A	B	A.B
0	0	0
0	1	1
1	0	1
1	1	1

OR from NAND gates

 


A	I	$\bar{A}$	B	II	$\bar{B}$	III	A+B
0	0	1	0	0	1	1	
0	0	1	1	1	0	0	
1	1	0	0	0	1	0	
1	1	0	1	1	0	0	

26

OR gates using NAND gates




OR

 

A	B	A.B
0	0	0
0	1	1
1	0	1
1	1	1

OR from NAND gates

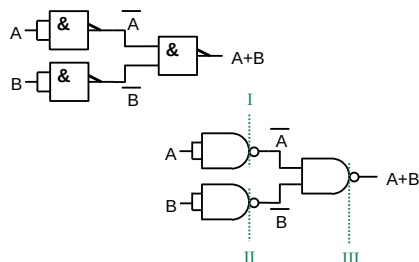


A	I	$\bar{A}$	B	II	$\bar{B}$	III	A+B
0	0	1	0	0	1	1	0
0	0	1	1	1	0	0	1
1	1	0	0	0	1	0	1
1	1	0	1	1	0	0	1

27

All gates using NOR gates




N/OT

 

Binary Truth table


A	B	A+B
0	0	0
0	1	1
1	0	1
1	1	1

AND

 

A	B	$\bar{A}$	$\bar{B}$	A.B
0	0	1	1	0
0	1	1	0	0
1	0	0	1	0
1	1	0	0	1

OR

 


A	B	$\bar{A+B}$	A+B
0	0	1	0
0	1	0	1
1	0	0	1
1	1	0	1

28

Exercise #1




 1. Draw the equivalent circuit for the following logic gates



7

 2. Draw the equivalent circuit for the following logic gates




29


Exercise #1



 1. Draw the equivalent circuit for the following logic gates



 2. Draw the equivalent circuit for the following logic gates




30

 Exercise #2



Draw the logic gate combination to represent the following circuit diagram



S2 button not pressed conducts, button pressed short-circuit so it acts like an inverter.




7

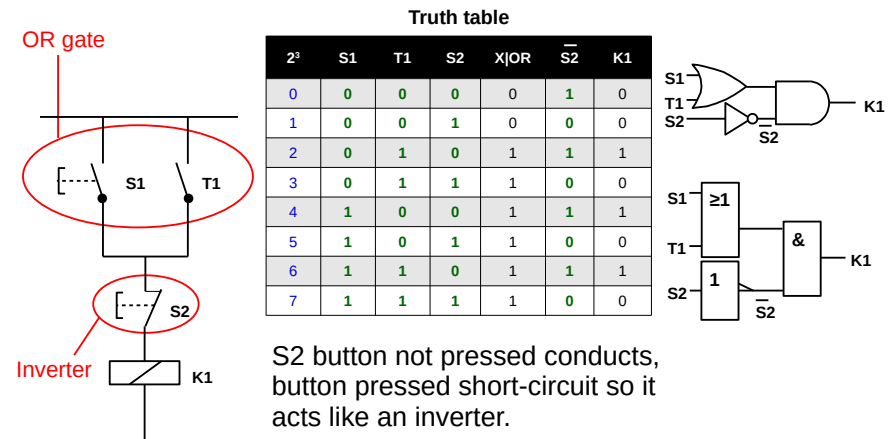Exercise #2



Draw the logic gate combination to represent the following circuit diagram




S2 button not pressed conducts, button pressed short-circuit so it acts like an inverter.

31


32



Programmable Logic Controller (PLC)

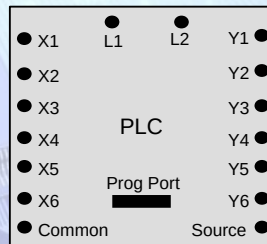

Programmable Logic Controller (PLC)

 


34


PLC



Power Supply & Rack

 

 Controller / Central Processing Unit (CPU)




Input/Output(I/O) Sub-System



35

PLC inputs

 

36

Ladder diagram features



- Power flows from left to right.
- Output on right side can not be connected directly with left side.
- Contact can not be placed on the right of output.
- Each rung contains one output at least.
- Each output can be used only once in the program.
- A particular input and/or output can appear in more than one rung of a ladder.
- The inputs and/or outputs are all identified by their addresses, the notation used depending on the PLC manufacturer.

37


Ladder Logic Function Block Diagrams



	Functional Block Diagram	Ladder Diagram	Program List
AND			<pre>LD X1 AND X2 OUT Y1 END</pre>
NOT			<pre>LDI X1 OUT Y1 END</pre>
OR			<pre>LD X1 OR X2 OUT Y1 END</pre>


38

Ladder Logic

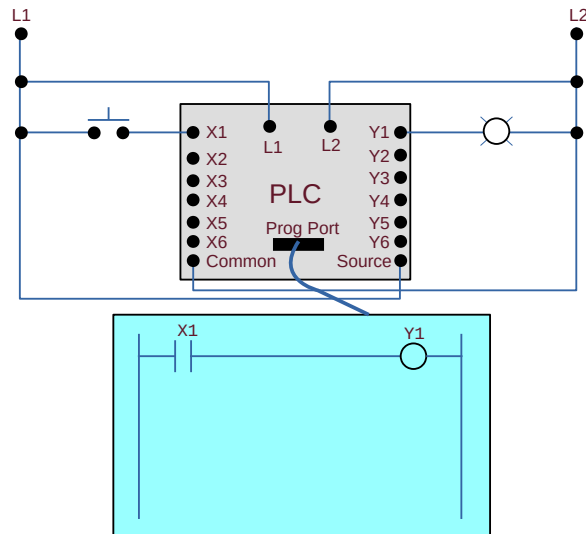

39

Ladder Logic

 


40

Ladder Logic



- Logical **AND**

 - Switch 1 AND Switch 2 must be pressed for current to flow to the motor




- Logical **AND** with N/OT

- Door switch 1 AND N/OT Obstruction to run the motor (to close door)



- Logical **OR**

 - Either the Inside OR the Outside switch must be depressed to activate motor




41

Ladder Logic




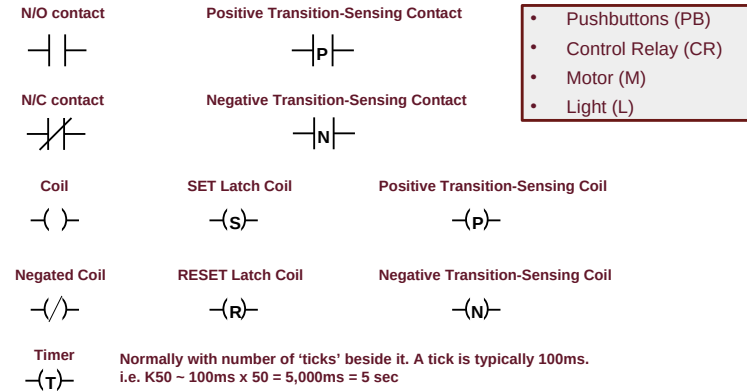- A programming language that represents a program via a graphical diagram based on the circuit diagrams of relay logic hardware.
- Ladder logic is used to develop software for PLCs used in industrial control applications.




42

Ladder Logic

 


- X2 is in a normally Closed state.

 


43

Ladder Logic

 


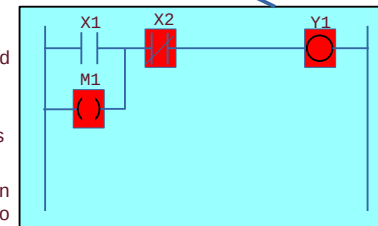- X1 is pressed to activate.
- Coil M1 is energised and voltage is applied to the motor Y1.
- X1 is released and returns to open state.
- Motor continues to run because M1 continues to power rung ("latching").




44

Ladder Logic

 


 - X1 is pressed to activate.
- Coil M1 is energised and voltage is applied to the motor Y1.




45

Ladder Logic

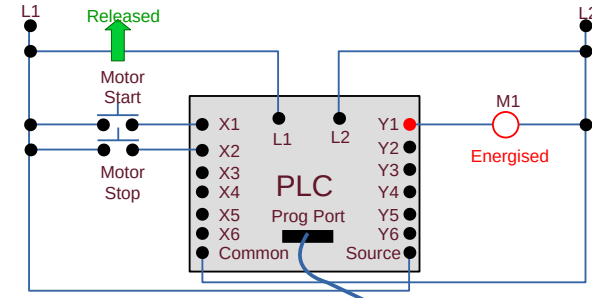


 - X1 is pressed to activate.
- Coil M1 is energised and voltage is applied to the motor Y1.
- X1 is released and returns to open state.
- Motor continues to run because 'seal-in' contact continues to power Y1.




46

Ladder Logic

 


 - X2 is actuated and then released.
- X2 changes to an open state breaking continuity to M1.
- X2 returns to Normally Closed state but motor does not start until X1 is actuated again.




47

Ladder Logic

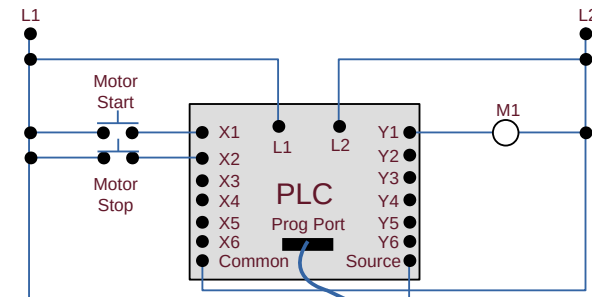

 - It is typical also that Control Relays (CR) are illustrated as N/O or N/C contact.
- Diagram is normally completed with a rung with END added as shown.




48



Instruction	Abbreviation
Load, Normally Open (N/O) contact	LD
Load, Normally Closed (NC) contact	LDI
AND; N/O contact in series	AND
AND; N/C contact in series	ANI
OR; N/O contact in parallel	OR
OR; N/C contact in parallel	ORI
Connect block in series	ANB
Connect block in parallel	ORB
Timer On Delay	TON
Timer Off Delay	TOF
Retentive Timer	RTO
Output	OUT

49

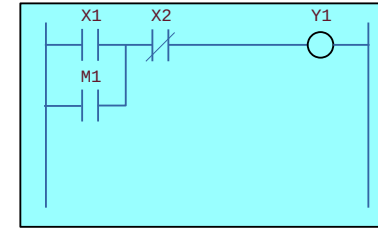

```

0  LD  X1    Load N/O contact on input X1
1  OR  M1    Define M1 Control Relay in OR block with X1
2  ANB -     Connect block to next block in series
3  LDI X2    Load N/C contact on input X2
4  OUT Y1    Current is supplied to motor on Y1
9  END
    
```

50

Exercise #1




1. Draw a ladder diagram represented by the following instruction list

```

0  LD  X0
1  OR  X1
2  ANB -
3  LD  X2
4  OR  X3
5  OR  X4
6  ANB -
7  ANI X5
8  OUT Y0
9  END
    
```

7

52

 

Exercise #1

PLC Ladder diagram


Exercise #1



 1. Draw a ladder diagram represented by the following instruction list

```

0  LD  X0
1  OR  X1
2  ANB -
3  LD  X2
4  OR  X3
5  OR  X4
6  ANB -
7  ANI X5
8  OUT Y0
9  END
    
```




53

Ladder diagram example



The figure and table represent a ladder diagram and the input/output schedule for a process.

 Draw a circuit diagram of the process and describe its operation.




Input / Output Schedule

Inputs			Outputs		
Device	Item desc	PLC term no	Device	Item desc	PLC term no
Stop PB	S1	X0	Siren	H1	Y0
Start PB	S2	X1			

54

Ladder diagram example

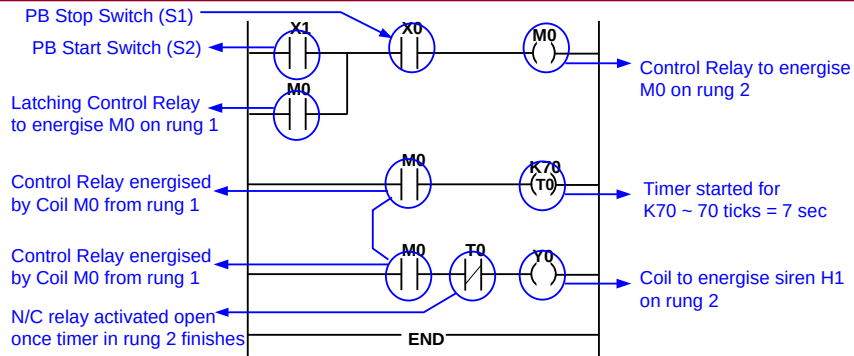


Input / Output Schedule

Inputs			Outputs		
Device	Item desc	PLC term no	Device	Item desc	PLC term no
Stop PB	S1	X0	Siren	H1	Y0
Start PB	S2	X1			


55

Ladder diagram example

 


56

PLC Power

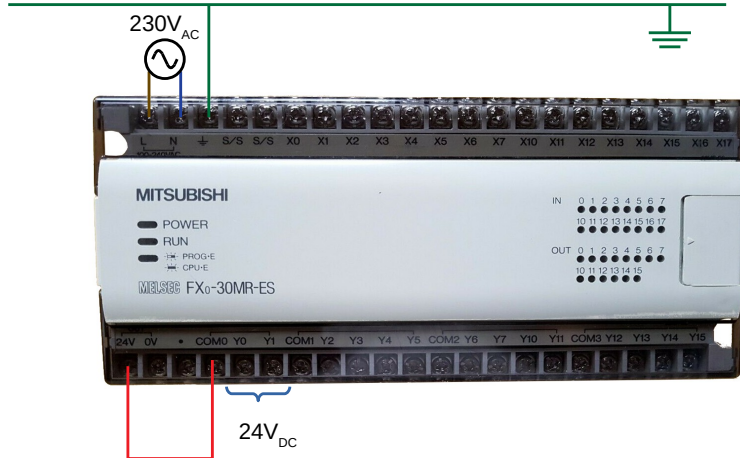


57

PLC Power

 


58

PLC Power

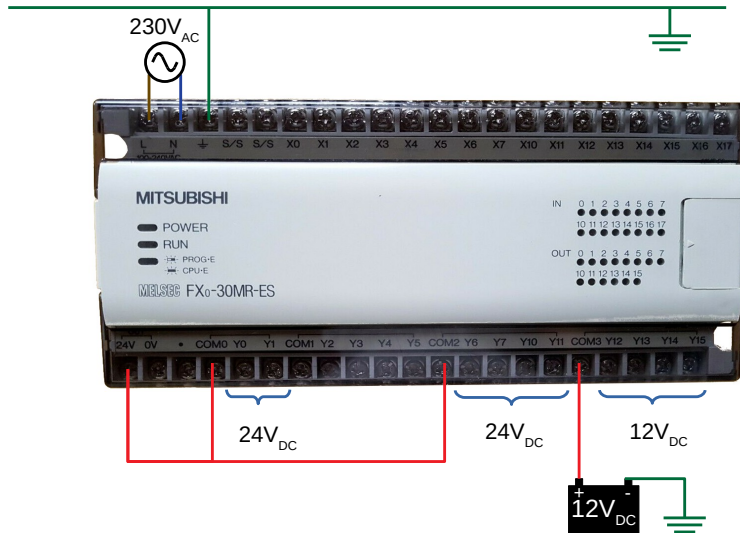

59


PLC Power

 

How would I get 48V_{DC} outputs here and 24V_{DC} everywhere else ?


60

PLC Power

 

61

PLC Power

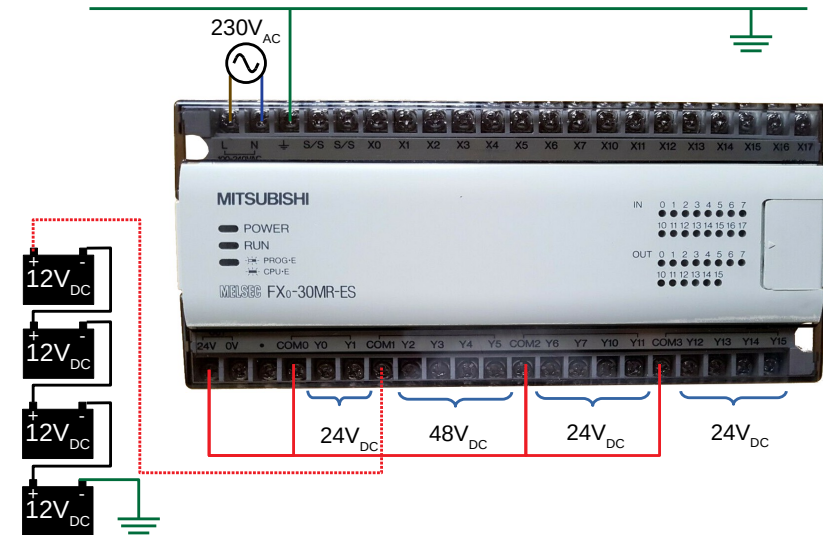


62

PLC Laboratory




Exercise #2 PLC Laboratory

 

230V mains light OK
All switches in UP position
24V connected to COM / 0 / 1
Y0 to Lamp Y0
X0 to Pushbutton X0

64

PLC Laboratory

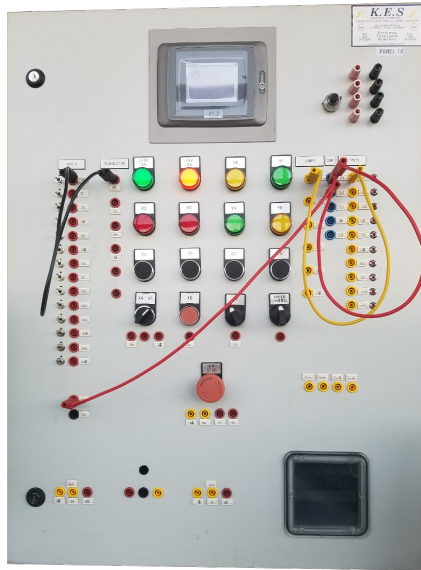

230V mains light OK
All switches in UP position
24V connected to COM /0 /1
Y0 to Lamp Y0
X0 to Pushbutton X0


65

GX Developer




66


GX Developer

 

New Project

 


Online → Transfer Setup

 



Baud rate: 9,600 b/s

67

Program #1

 

New Project

  

- Convert → Convert (Compile program)
- Online → Write to PLC

68

Program #1



- Press button X0, what happens ?

69

Program #1



- Press button X0, what happens ?
- What happens when you release ?



70

Program #1




- Press button X0, what happens ?
- What happens when you release ?



71

Program #2

 

- Convert → Convert (Compile program)
- Online → Write to PLC

- What do you think the latch does ?

72

Program #2



- Press button X0, what happens ?

73

Program #2



- Press button X0, what happens ?
- What happens when you release ?



74

Program #2



- Press button X0, what happens ?
- What happens when you release ?
- Why ?



75

Adding an additional button



- Connect X1 to X1 pushbutton



76

Program #3



- Convert → Convert (Compile program)
- Online → Write to PLC

77

Program #3



- Press button X0, what happens ?

78

Program #3



- Press button X0, what happens ?



- What happens when you release ?

79

Program #3



- Press button X0, what happens ?

- What happens when you release ?



- Why ?

- Press button X0 again, what happens ?

- Why ?

80

Program #3



- Press button X0, what happens ?
- What happens when you release ? 
- Why ?
- Press button X0 again, what happens ? 
- Why ?

81

Program #3




- Press button X1, what happens ?
- What happens when you release ? 
- Why ?
- Press button X1 again, what happens ?
- Why ?

82

Adding an additional button



 - Connect X2 to button X2 with a black wire.



83

Program #4



- Convert → Convert (Compile program)
- Online → Write to PLC

84

Program #4



- Press button X0, what happens ?



- Press button X1, what happens ?




- Press button X2, what happens ?



85

Program #5

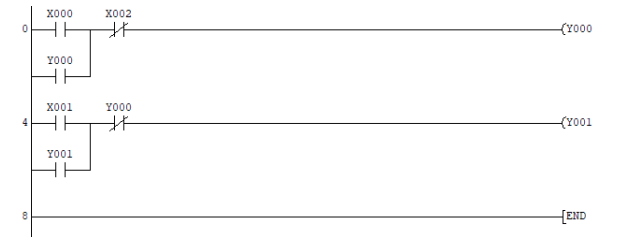

- Convert → Convert (Compile program)
- Online → Write to PLC

86

Program #5



Press button X0



Press button X1



Why doesn't Y1 light ?

87

Program #5



Press button X0



Press button X1



Press X2




Why did Y0 extinguish ?

88

Program #5



Try this sequence and explain

 

89

Instruction Set



- View → Instruction List (Alt+F1)



```

0 LD X000
1 OR Y000
2 ANI Y001
3 OUT Y000
4 LD X001
5 OR Y001
6 ANI Y000
7 OUT Y001
8 END
    
```

Instruction	Abbreviation
Load, Normally Open (N/O) contact	LD
AND; N/C contact in series	ANI
OR; N/O contact in parallel	OR
Output	OUT

90

Exercise #3.1

  

- Build a PLC circuit to control the filling of the liquid tank.
- Draw a ladder diagram to control the supply and output of the liquid.

92


Exercise #3

Liquid tank

Exercise #3.1



- Implement program on PLC.

 

93

Exercise #3.2




- Adjust the program so the button can be pressed once and the fill will continue or the output will continue.

 Exercise #3.2



- Adjust the program so the button can be pressed once and the fill will continue or the output will continue.



95



Exercise #3.2



- Adjust the program so the button can be pressed once and the fill will continue or the output will continue
- What is the flaw with this ?

96

Exercise #3.3

  


- Add a Stop button
(Stop buttons are physically N/C push-buttons by default and therefore need to be Examine-ON so in the ladder diagram it appears NO).

97

 Exercise #3.3





- Adjust the program so the button can be pressed once and the fill will continue or the output will continue.



98



Exercise #3.4

 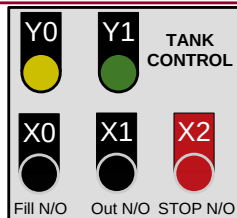

- Add visual indicators for the fill and output states.

99

Exercise #3.5

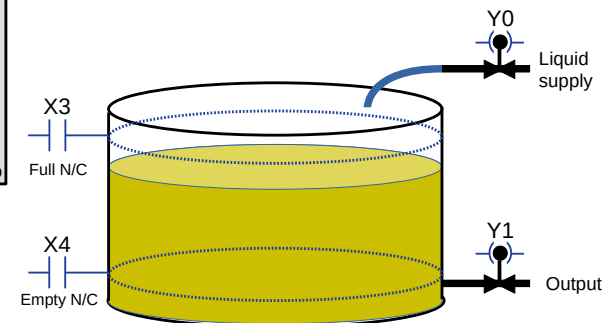 


- The liquid in the tank cannot empty below the output pipe
- The liquid in the tank cannot over fill either, two sensors are added
- Include these in the program to prevent overflow or the tank emptying.

100

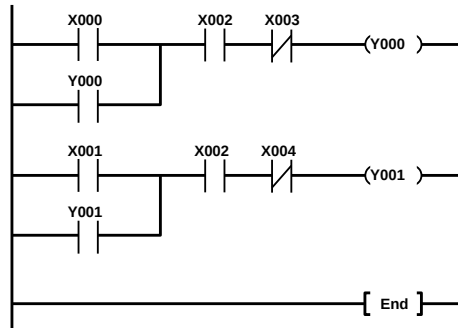Exercise #3.5



- Adjust the program so the button can be pressed once and the fill will continue or the output will continue.



101

Exercise #3.5



- Show the associated Instruction List.

0	LD	X000	(Fill switch)
1	OR	Y000	(Tap latch)
2	AND	X002	(Stop switch)
3	ANI	X003	(High level sensor)
4	OUT	Y000	(Tap actuator)
5	LD	X001	(Drain switch)
6	OR	Y001	(Drain latch)
7	AND	X002	(Stop switch)
8	ANI	X004	(Low level sensor NC)
9	OUT	Y001	(Drain actuator)
10	END		(End)

102

Learning outcomes



- Logic Circuits ✓
- PLC Operating Principles ✓
- PLC Control Features ✓
- Ladder Diagrams ✓

103

